

SER 232




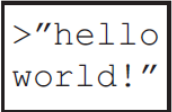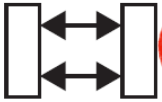
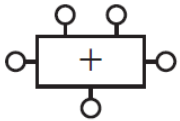

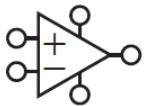


Computer Systems Fundamentals I

Topics

- Design & Abstraction Levels
- Data vs. Control

Higher-Level Design

- Transistor-level design
- Logic-level design
 - Logic gates made up of transistors
- Register-transfer level (RTL) design
 - Datapath components made up of logic gates

Application Software		Programs
Operating Systems		Device Drivers
Architecture		Instructions Registers
Micro-architecture		Datapaths Controllers
Logic		Adders Memories
Digital Circuits		AND Gates NOT Gates
Analog Circuits		Amplifiers Filters
Devices		Transistors Diodes
Physics		Electrons

Data vs. Control

- Data:
 - A value that comes from the datapath (registers) or other devices:
 - Buttons
 - Sensors
 - Memory (RAM)
 - Secondary storage (HDD or SSD)

Data vs. Control

- Control:
 - Indicates what do with data
- Source:
 - Custom processor:
 - Determined by controller (current state and inputs)
 - General purpose microprocessor:
 - Control signals dictated by program instructions

Data vs. Control

- Analogy: TV
 - Control: Remote gives control (volume, channel, brightness, ...)
 - Data: Content of channel (video, audio)

Datapath Components

- Data storage
 - Registers
- Data manipulation
 - Boolean and arithmetic operations

SER 232

Computer Systems Fundamentals I

Topics

- Datapath Components: Data Storage

Register

- Storage device for multiple bit values
 - Bus input for storing a new value
 - Bus output for reading currently stored value
- Usually stores data if the clock input sees a *rising edge*

Parallel-Load Register


- The *load* control line is equivalent to Logisim register's *en* (enable) pin
 - Method for preventing clock ticks from updating the register value
 - Gives control over when the register is supposed to store values
 - $en = 0$ means the register will retain stored value, independent of rising edges from clock and changed input values

Register Files

- A collection of registers
- Separate control inputs for reading and writing to:
 - Select a register to read/write from/to
 - Enable access to write and/or read
- Uses multiplexer to route data from selected register to output
 - Register file can have only 1 output but several registers to store data in and load from

Register File Example

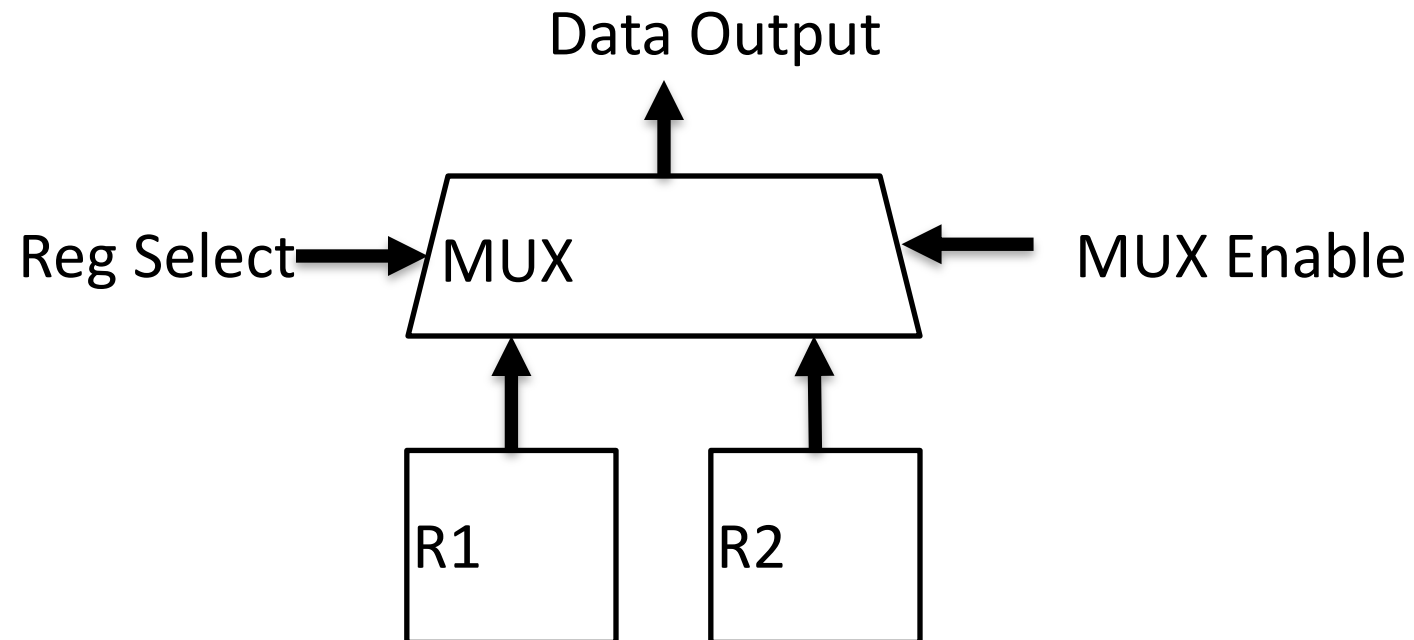- Example for the reading part of a register file



Logical Shift Right

- Suppose we want to shift the value 0110_2 to the right once
 - Programming example:
`y = 0b0110 >> 1`

0	1	1	0
---	---	---	---


Logical Shift Right

- Each bit is moved right one position

0	1	1	0
---	---	---	---

Logical Shift Right

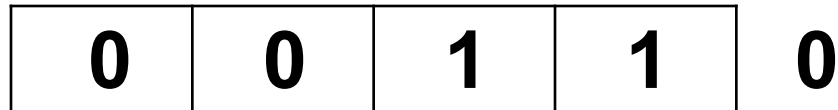- Least significant bit is removed
- Most significant bit become a zero



Logical Shift Right

- The original value: $0110_2 = 6_{10}$
- The new value: $0011_2 = 3_{10}$
 - Shifting right is equivalent to dividing by 2


0	0	1	1
---	---	---	---

Logical Shift Left

- Same process as shifting right
 - Each shift to the left is equivalent to multiplying by 2
 - Programming example:
 $y = 0b0110 \ll 1$
 - Shifting result:
 $y = 0b1100$

Shift Registers

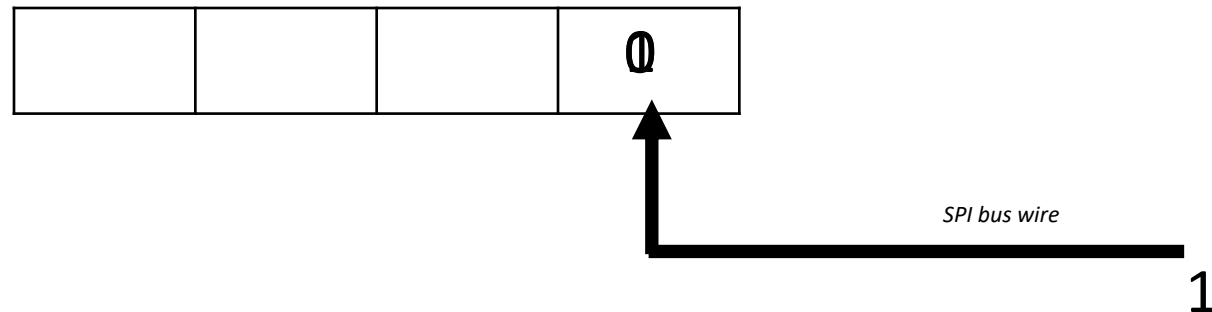- A register with a control inputs that causes the stored value to be shifted
 - E.g. shift register is used for a communication bus called SPI (serial peripheral interface), which transmits bits using 1 wire (1 bit at a time)



Shifters

- Shifting can also be done by components that do not include a register
- More sophisticated shifters, such as a barrel shifter, can shift by a specified number of bits
 - $x = x \ll 4$

SER 232


Computer Systems Fundamentals I

Topics

- Datapath Components: Data Manipulation

Adders

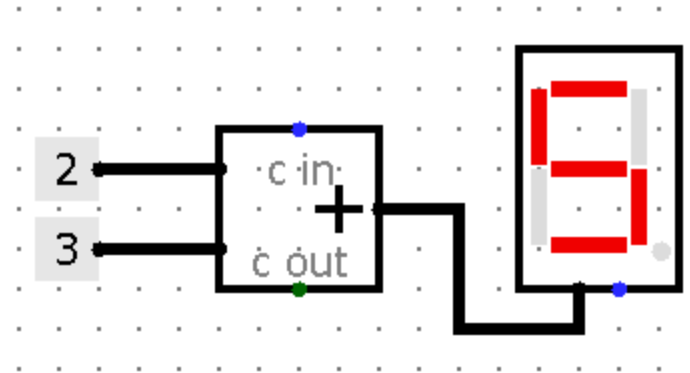- Component adds two inputs (and a carry)
 - Outputs result and a carry bit




Adder: Ripple-Carry Style

- Half adder:
 - Two 1-bit number inputs
 - Result and carry output
- Full adder:
 - Two 1-bit number inputs and a carry input
 - Result and carry output

Adder: Ripple-Carry Style

- N bit adder made up of N-1 full adders (FA) and a single half adder (HA)
 - Each adder handles a specific bit position
 - Carry out of each adder goes to the next higher bit position adder
 - HA used in LSB where it doesn't need a carry input

Adder: Ripple-Carry Style

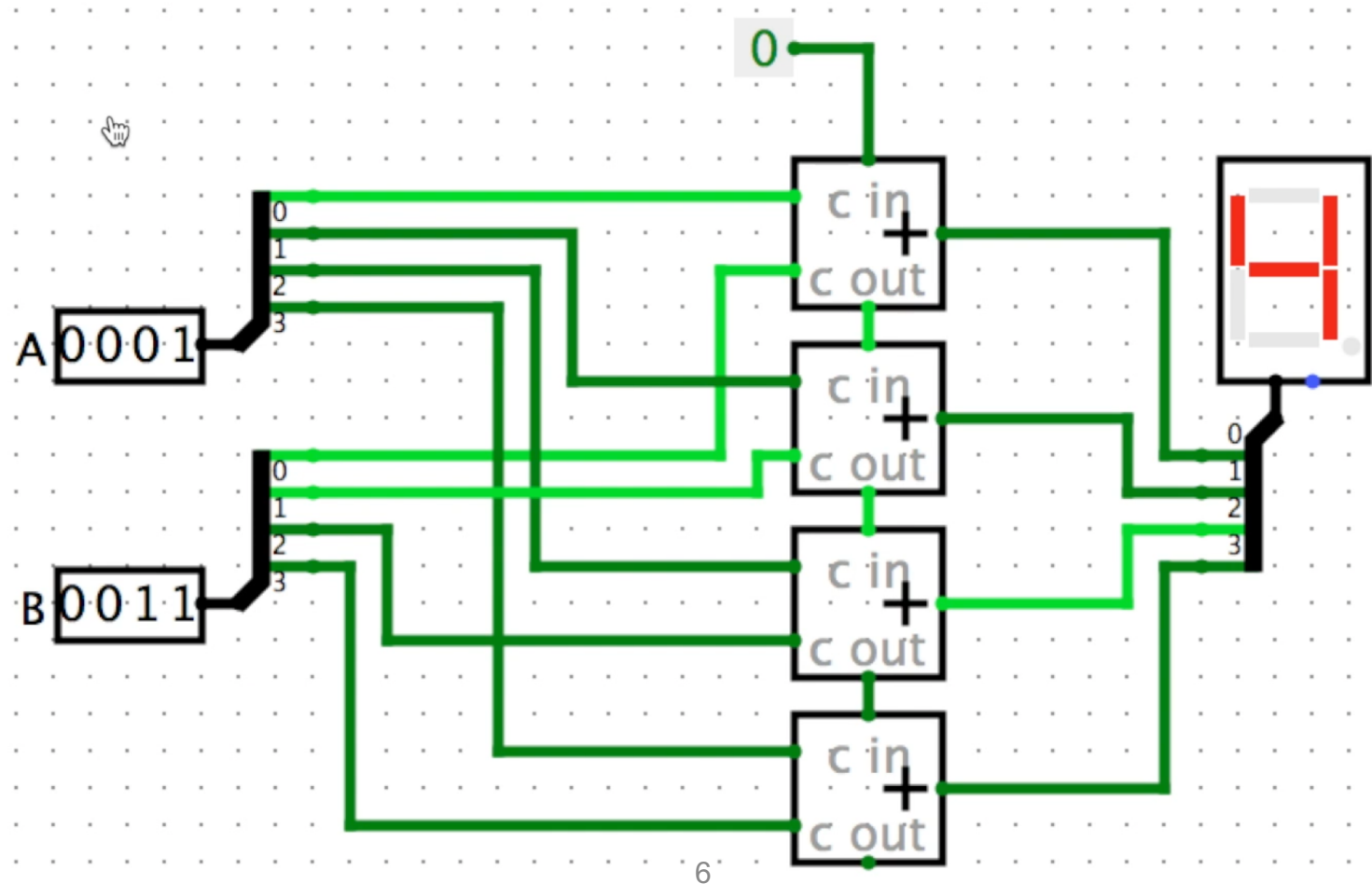


Subtraction

- Logisim subtraction similar to adder, but has borrow (b) in and out



$$\begin{array}{r} 0010 \\ - 0001 \\ \hline = 0001 \end{array}$$

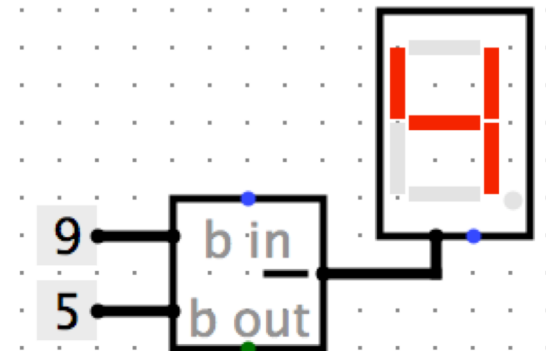- Position 0: We are performing 0b0 minus 0b1, which does not work
 - We have to borrow a 0b1 from position 1 to perform 0b10 minus 0b1, which results into 0b1
 - Borrowing 0b1 from position 1 will turn it from 0b1 to 0b0




Multiplier & Divider

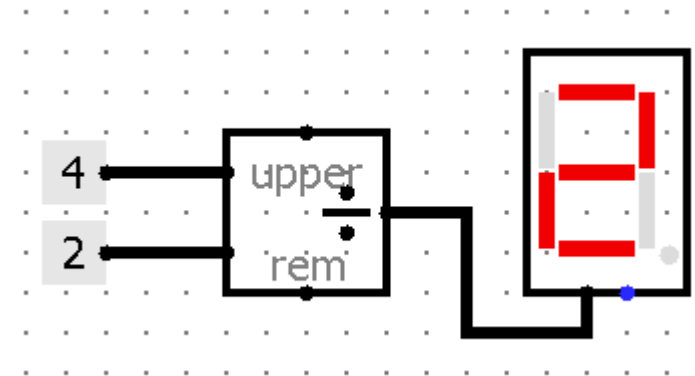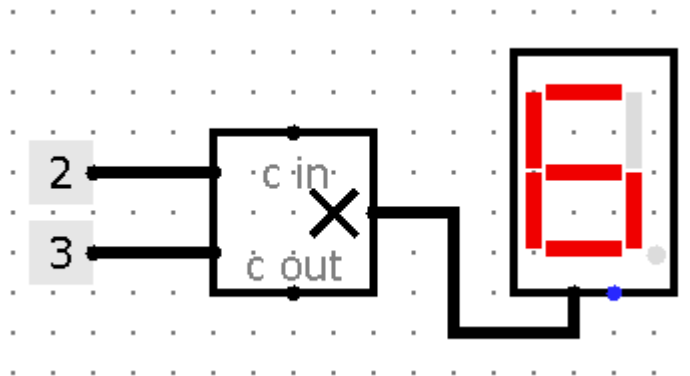- Component multiplies / divides two inputs
 - Outputs result



Comparators

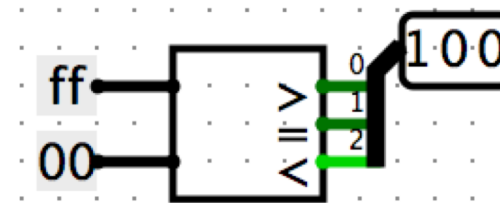- Equality
 - Are two inputs the same?
- Inputs A and B , and 3 Boolean outputs:
 - $A > B$
 - $A = B$
 - $A < B$



ALU

- Arithmetic Logic Unit
 - Merges multiple arithmetic operator components into a single component
 - Simplifies datapath layout

