

Sequential Circuits

Module 5

UGTA - Corey Lancelotta



Key Takeaways

Combinational vs. Sequential Circuits

Memory vs. No Memory

SR Latch

Problem: Oscillation

Level-Sensitive SR Latch

Problem: Avoiding $SR = 11$

D Latch

Problem: Clock Dependence

D Flip-Flop

Problem: Resource Heavy

Registers

Collection of D Flip-Flops


SEQUENTIAL

1. Output depends on **inputs and previous states**
2. Can store values (**memory**)
3. **Goal:** We need to figure out a way to store a value **without permanently storing** the value

COMBINATIONAL

 
1. Output depends **only on inputs**
2. Can't store values (**no memory**)

We can't change the value of F after initially setting the value!



DETAILS

 1. Introduces a **feedback mechanism**
2. **Cross Coupling**: The output of each NOR gate serves as an input to the other NOR gate
3. $SR = 00$ is "**undefined**" without knowledge of the previous state



S	R	t	Q
0	0	*	*
0	1	1	0
1	0	0	1
1	1	0	0


* Unknown without knowledge of previous state

SOLUTION & PROBLEM

1. **SOLUTION**: Allows us to **store a value AND change it**
2. **PROBLEM**: **Oscillation** occurs when the input changes from $SR = 11$ to $SR = 00$. (We must prevent $SR = 11$)

DETAILS

 1. Introduces a mechanism to **regulate when the SR values enter the latch**
2. **Enable Input, C**: The latch receives changes in SR values only when $C = 1$
3. We still need to **design a way to ensure that $SR = 11$ does not get sent to the latch**
4. $S1$ and $R1$ can change **only when $C = 1$**




SOLUTION & PROBLEM

1. **SOLUTION**: Allows us to **regulate when SR values are passed into the latch**
2. **PROBLEM**: Regulating SR values before entry into the latch **can be a burden** (We are essentially just relocating the problem)

D LATCH

DETAILS

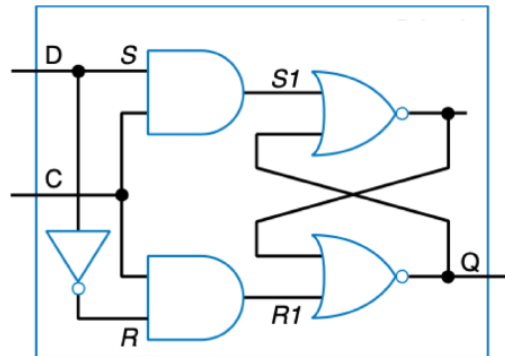1. Introduces a mechanism to ensure $SR = 11$ can't occur
2. The value of R will always be the opposite of S
3. Still uses the enable input, C




SOLUTION & PROBLEM

1. SOLUTION: Relieves the burden on regulating SR values prior to entry into the latch
2. PROBLEM: When chaining D Latches together, the number of latches that are triggered is dependent on the clock signal

DETAILS

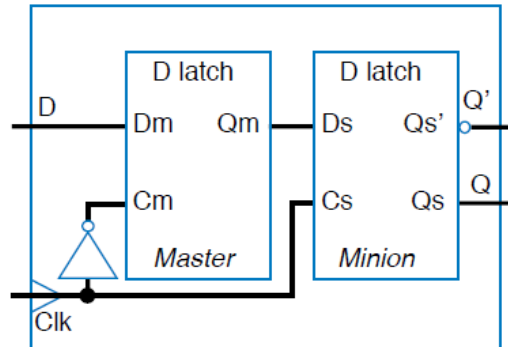1. Introduces a mechanism to ensure that storing values is independent of the clock signal
2. Uses 2 D Latches: Master and Minion
3. Storing values is edge-triggered
4. Master is enabled when $\text{Clk} = 0$
5. Minion is enabled when $\text{Clk} = 1$




SOLUTION & PROBLEM

1. SOLUTION: Removes the dependence on the clock signal
2. PROBLEM: Uses a lot of components (resource heavy)

LATCH OVERVIEW


SR Latch

 

FEATURE: Store and change stored values

PROBLEM: Oscillation


Level-Sensitive SR Latch

 

FEATURE: Regulate when SR values enter the latch

PROBLEM: Burdensome to manage SR values


D Latch

 

FEATURE: Relieves burden of managing SR values

PROBLEM: Clock frequency dependence

D Flip-Flop

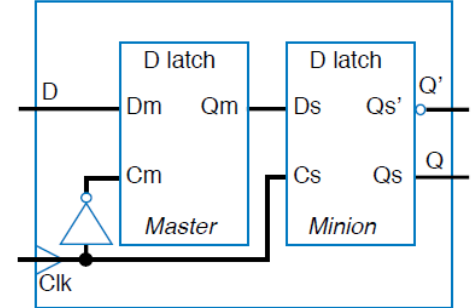


FEATURE: Clock frequency independence

PROBLEM: Resource heavy

DETAILS


 
1. Combines multiple D Flip-Flops
2. All latches share a single clock signal





Practice Problems Questions

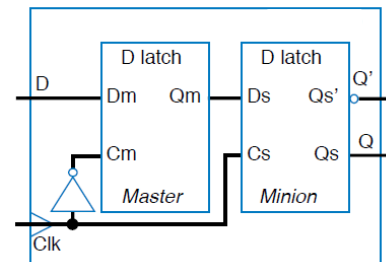 1. In the **SR Latch** to the right, what are the values of **t** and **Q** when **SR = 10**?
2. In the **SR Latch** to the right, what are the values of **t** and **Q** when **SR = 01**?
3. In the **D Flip-Flop** to the right, what is the value of **Qm** when **D = 1** and **Clk = 1**?
4. In the **D Flip-Flop** to the right, what is the value of **Qm** when **D = 0** and **Clk = 0**?
5. Why is it an issue for **D Latches** to be **dependent on the frequency** of the clock signal?
6. (**True or False**) In a chain of D Flip-Flops, a **high clock frequency** could cause **zero** D Flip-Flops from storing a value?
7. (**True or False**) In a chain of D Flip-Flops, a **short clock period** could cause **zero** D Flip-Flops from storing a value?





Practice Problems **Answers**

1. $t = 0$ and $Q = 1$
2. $t = 1$ and $Q = 0$
3. **Impossible to tell** without knowledge of the previous state. The value stored in Q_m will update with the value of D only when $Clk = 0$.
4. $Q_m = 0$
5. The **frequency of a CPU is variable**. Therefore, if the circuit behavior is dependent on the frequency, **we can't be certain** that the circuits we create will always exhibit the desired behavior.
6. **Yes!** A high frequency means the clock period is shorter. This short clock period could be too short to fully trigger the first D Flip-Flop.
7. **Yes!** A short clock period could be too short to fully trigger the first D Flip-Flop (same behavior as previous question)!