SER 232 Quiz 2 Book Practice Problems Solution

• 2.32: F = (ab' + b)'

• 2.33: F = (ab' + b) + a'c

2.35:

a)	а	b	С	F	
	0	0	0	1	
	0	0	1	1	
	0	1	0	1	
	0	1	1	1	
	1	0	0	0	
	1	0	1	0	
	1	1	0	1	
	4	4	4	_	

a	b	С	F	c)	а	b	С	F
0	0	0	1		0	0	0	1
0	0	1	1		0	0	1	0
0	1	0	1		0	1	0	1
0	1	1	1		0	1	1	0
1	0	0	0		1	0	0	1
1	0	1	0		1	0	1	1
1	1	0	1		1	1	0	1
1	1	1	0		1	1	1	1

b)	а	b	с	F
	0	0	0	1
	0	0	1	1
	0	1	0	1
	0	1	1	1
	1	0	0	1
	1	0	1	1
	1	1	0	1
	1	1	1	1

d)	а	b	С	d	F
	0	0	0	0	1
	0	0	0	1	0
	0	0	1	0	1
	0	0	1	1	0
	0	1	0	0	1
	0	1	0	1	0
	0	1	1	0	1
	0	1	1	1	1
	1	0	0	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	0	1	1	0
	1	1	0	0	1
	1	1	0	1	0
	1	1	1	0	1
	1	1	1	1	0

2.43:

Inputs			Outputs		
	a	b	F		
	0	0	1		
	0	1	0		
	1	0	0		
	1	1	0		

• 2.44:

	Inputs				Outputs
a	b	c	ab' + b	a'c	F
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	0	1

2.48:

- a) F(a, b, c) = a'bc + abc' + abc
- b) F(a, b, c) = a'bc' + a'bc
- c) F(a, b, c) = a'b'c + a'bc' + a'bc + ab'c' + abc' + abc'd) F(a, b, c) = a'b'c' + a'bc' + ab'c' + abc'