

Example

Design a sequence detector that detects a sequence of 2 zeros or 3 ones on an incoming serial data line. Assume an asynchronous reset that initializes the machine.

Let the input be x , and the output be z .

We have the following state diagram

