

Gate Delay & Clocks

Module 4

UGTA - Corey Lancelotta



Key Takeaways

Gate Delay

Characterizing Circuits

Timing Diagrams

Identifying Intermediate Values

Clocks

Calculating Periods and Frequencies

GATE DELAY

Longest Path


- A theoretical “upper bound” on the delay of a circuit.
- The greatest number of gates from any input to any output.

Shortest Path

- A theoretical “lower bound” on the delay of a circuit.
- The least number of gates from any input to any output.

Useful Notes

 - Longest Paths and Shortest Paths are unrelated to specific input changes and unrelated to Timing Diagrams.
- You can rule out some inputs by noticing that another input will include more or less gates. (For example, the longest path will never include Input B, since a path including Input A will always be longer)



GENERAL CONCEPTS

1. Gates require time to “process” their inputs
2. Assumptions made in the context of this course:
 - All gates have identical delays
 - Wires do not have delays
3. Longest Path and Shortest Path are “properties” of a circuit as a whole


Setting up the Timing Diagram

1. Identify all **Inputs**, **Outputs**, and **Intermediate Variables**
2. Identify the **initial values** of all of these variables

Identifying Synchronous Gate Delays

 1. When a wire changes value, **follow the wire to ALL gates**
2. Any and all gates (no matter how long the wire is) you reach will introduce **simultaneous gate delays**

For Example: In the following circuit diagram, the delays from gates **2, 3, and 5** occur **simultaneously** after the input changes from $AB = 10$ to $AB = 11$




DON'T FORGET

1. Timing Diagrams describe the dynamic behavior of a circuit given a change of state. There is **no single timing diagram** for a circuit
2. We are assuming that all gates have **identical** delays and that wires **do not** have delays
3. Timing Diagrams are a **separate concept** from Longest/Shortest Paths
4. Logisim's **wire coloring** can be very helpful in identifying initial and intermediate values

Describing the Clock Signal

 1. Rising Edge
2. Falling Edge
3. Period
4. Takes a value of 0 or 1



Converting between Period and Frequency

1. Convert to base units (Hz and seconds)
2. Use the $\text{Period} = 1 / \text{Frequency}$ relationship
3. Convert to the requested units

Pico (p)	10^{-12}
Nano (n)	10^{-9}
Micro (μ)	10^{-6}
Milli (m)	10^{-3}

Kilo (K)	10^3
Mega (M)	10^6
Giga (G)	10^9
Tera (T)	10^{12}

DON'T FORGET

1. Converting to base units (Hz and seconds) first is often a fool proof method
2. Clocks can be used to synchronize circuits
3. Clocks are the solution to Gate Delay
4. $\text{Period} = 1 / \text{Frequency}$




Practice Problems **Conversions**

1. Convert the **Frequency of 200 Hz** to a **Period in nanoseconds**.
2. Convert the **Frequency of 490 kHz** to a **Period in picoseconds**.
3. Convert the **Frequency of 4.5 GHz** to a **Period in seconds**.
4. Convert the **Frequency of 0.1 MHz** to a **Period in microseconds**.
5. Convert the **Period of 500 nanoseconds** to a **Frequency in MHz**.
6. Convert the **Period of 4,500 microseconds** to a **Frequency in Hz**.
7. Convert the **Period of 24 seconds** to a **Frequency in GHz**.
8. Convert the **Period of 60,000 picoseconds** to a **Frequency in MHz**.



Practice Problems **Timing Diagram**

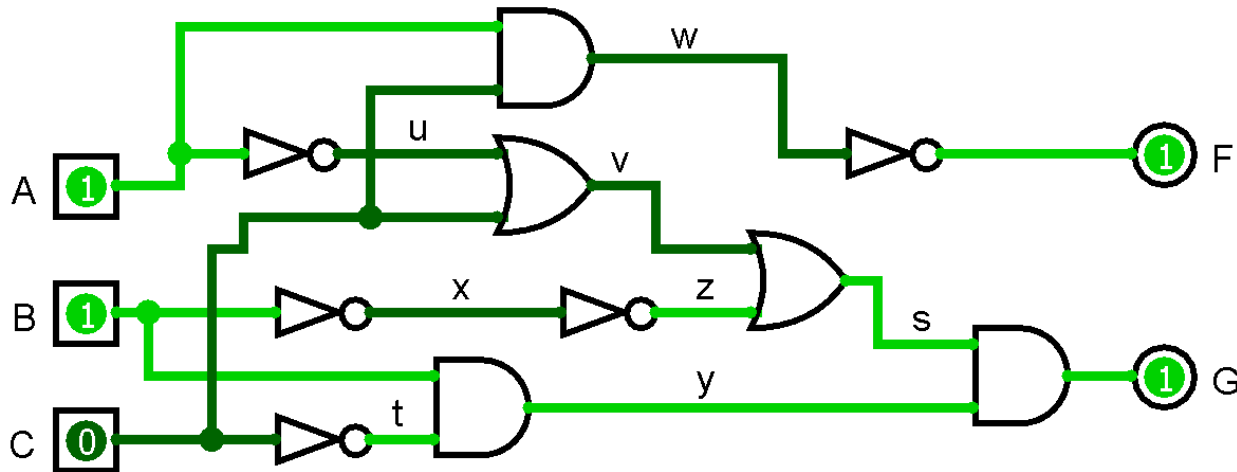9. What is the **longest path** and **shortest path** in the following circuit?
10. Create a **Timing Diagram** for the following circuit's input change of **ABC = 110** to **ABC = 100**.






Practice Problems **Answers**

1. 5×10^6 ns
2. 2.04×10^6 ps
3. 2.22×10^{-10} s
4. 10 μ s
5. 2 MHz
6. 222.22 Hz
7. 4.17×10^{-11} GHz
8. 16.67 MHz



Practice Problems **Answers**

 9. Longest Path = **4 Gate Delays**
Shortest Path = **2 Gate Delays**





Practice Problems **Answers**

10.

	Initial State	delay 1	delay 2	delay 3	Final State
A	1 0				1 0
B	1 0				1 0
C	1 0				1 0
s	1 0				1 0
t	1 0				1 0
u	1 0				1 0
v	1 0				1 0
w	1 0				1 0
x	1 0				1 0
y	1 0				1 0
z	1 0				1 0
F	1 0				1 0
G	1 0				1 0