

SER232 - Assignment 7

[10 Points]

Description

This assignment covers the datapath components: *Register File* and *ALU*. You are supposed to create a custom register file that can store up to 4 different values using registers, and output two of the stored values. Those two numbers are then passed into a custom ALU that calculates the result of one of eight possible operations. Key aspect of this assignment is to understand how to control registers, how to utilize logic components and how to design a custom ALU.

Tasks

Use the provided template to implement your custom *register file* and *ALU*.

Register File

The register file must fulfill the following requirements and functions:

- The register file must be able to store four different 4-bit numbers.
- With every rising edge of the clock, the register file will store the current input value into the selected register. The *write select* input is used to determine where this value will be stored. For each possible input value of *write select*, a different register is being selected.
- This custom register file has two 4-bit outputs: *number 1* and *number 2*. Using the *num 1 select* and *num 2 select* inputs, the user can select two of the four stored values that will be used as output value (separately for each of the two outputs). It is possible to select the same value for both outputs.

Notes:

- You are allowed to (and should) use the built-in logic components provided by Logisim. Think about the storing and retrieving part separately, review the function of all logic components we covered, and find the component(s) that allows you to implement the required function of the register file. You do not have to create a circuit on your own and can implement the entire register file by utilizing the correct logic components with the provided inputs and outputs.
- The *clear* input of the register should not be used (do not connect anything to it). However, the *enable* input is a very important input for this assignment: It allows you to disable the register (*enable input* = 0), so it will keep the currently stored

value and ignores rising edges. Only if the register is enabled (*enable input = 1*) it will store the current input with the next rising edge.

- Remember to generate rising edges (toggle the clock input) for testing. Otherwise the registers will not store anything.

Custom ALU

Use the empty ALU subcircuit in the template to implement your ALU. You do not have to create additional subcircuits to do this. The ALU has a total of three inputs: first number, second number (coming from your *register file*) and select operation input. And one output: result. The first and second number are used as input for the operations the ALU performs. The select input decides which operation result will be the output value of the ALU. The ALU is supposed to calculate: *number 1* OPERATION *number 2*. The ALU must be able to compute signals with a 4-bit width. Make sure to add labels to all inputs and outputs (choose your own descriptive labels).

The following operations (*OP* input of ALU) should be performed for each binary select input combination:

- **000**: Addition
- **001**: Subtraction
- **010**: Multiplication
- **011**: Division
- **100**: Logic Bitwise AND
- **101**: Logic Bitwise OR
- **110**: Logic Bitwise XOR
- **111**: Logic Bitwise NOR

Notes:

- You are allowed to use the built-in arithmetic components and logic components provided by Logisim.
- You can change the inputs bit width / data bits of any gate to more than 1-bit. This will apply the logic operation bitwise and allow you to do this operation with a single gate.
- If the result is larger than 4 bits, it will be truncated (only 4 LSB will be shown). This behavior is intended for this assignment. Also, negative results do not have to be considered. Test your circuit with values within the possible range (positive values that can be represented with 4 bits).

Once you have implemented the ALU circuit, connect the wires in the *Datapath* circuit properly and test all operations of your ALU in combination with the register file. It is recommended to test the *register file* and *ALU* separately first and then test both in combination in the *Datapath* circuit.

Make sure the Logisim clock is running before you test the *Datapath* circuit (*Simulate, Ticks Enabled*; you can also increase the *Tick Frequency* to 64 Hz to make the circuit responds faster).

Deliverables

Important:

- Do not modify the template by moving or removing existing elements or wiring. Removing or moving elements given in the template can result into errors and make the circuit not work correctly. Points will be deducted if the existing elements in the template are modified. Moving existing elements is not necessary to finish this assignment. Only wiring the ALU in the main circuit components is allowed.
- Using the tunneling feature of Logisim is not allowed.

The following deliverables must be submitted on Canvas before the due date (see Canvas) as a single submission:

1. Your Assignment 7 Logisim circuit file, name: *lastname_a7.circ*