

# SER 232

Computer Systems Fundamentals I

# Topics

- MSB
- LSB

# MSB

- MSB stands for “Most Significant Bit”
  - MSB: Bit that has the highest value in binary number
    - E.g.: 1111; MSB has value of decimal 8
    - Usually MSB is the leftmost bit in binary number

# LSB

- LSB stands for “Least Significant Bit”
  - LSB: Bit that has the lowest value in binary number
    - E.g. 1111; LSB has value of decimal 1
  - Usually LSB is the rightmost bit in binary number
    - This is also called “LSB 0”: LSB is bit position 0
- Sometimes binary numbers are written in different order (LSB left, MSB right)
  - This is also called “MSB 0”: MSB is bit position 0

# SER 232

Computer Systems Fundamentals I

# Topics

- Logic Component: Multiplexer


# Logic Components

- Logic Components:
  - ... have a specific function and purpose
  - ... are made out of Logic Gates
- Most important / common components that we will look at:
  1. Multiplexer
  2. Demultiplexer
  3. Encoder
  4. Priority Encoder
  5. Decoder

# Logic Components

- Notation: Usually the amount of inputs and outputs of logic component is indicated in name
  - AxB <logic component name>
  - A = number of inputs
  - B = number of outputs
- E.g. 4x2 means 4 inputs; 2 outputs
  - “2x1 multiplexer” (2 in, 1 out)
  - “1x4 demultiplexer” (1 in, 4 out)

# Multiplexer

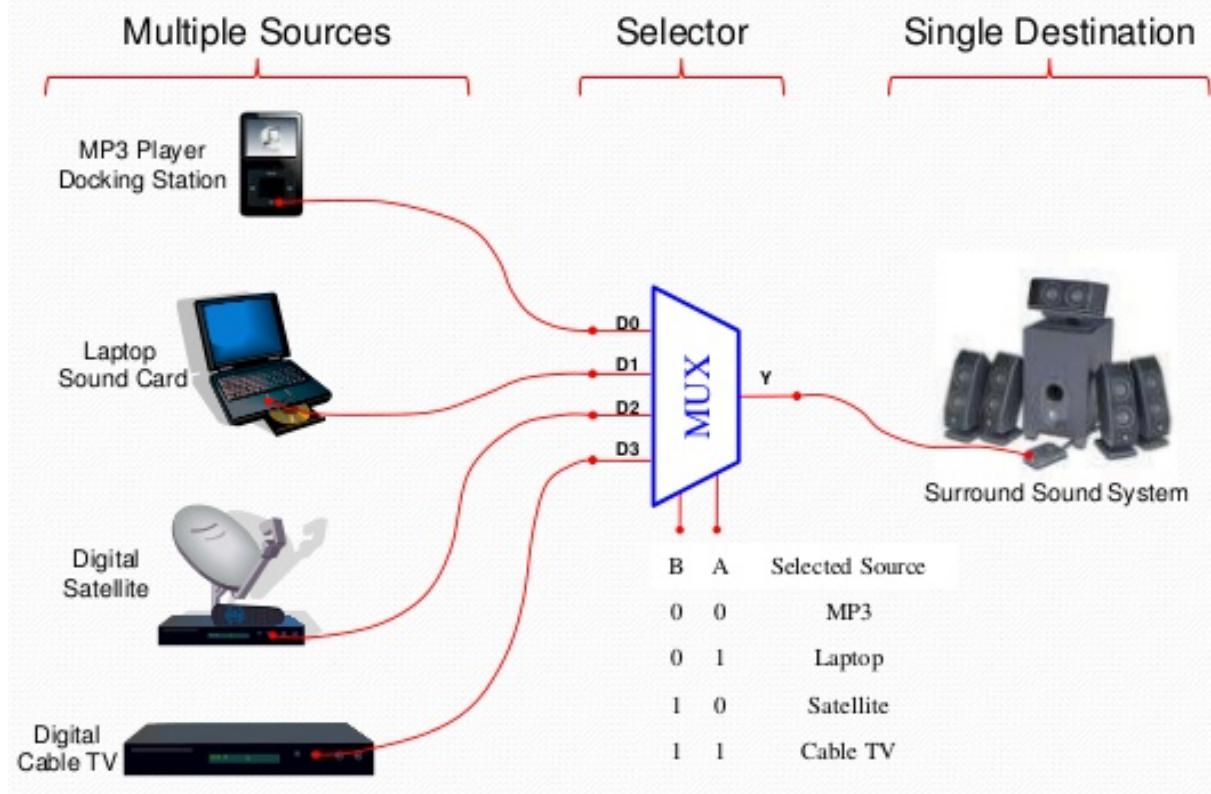


# Multiplexer

- Multiple sources to single destination
- Analogies:
  - AV receiver
    - Connecting multiple devices (consoles, satellite, Blu-ray) output to one TV or one speaker system
  - Vehicle speedometer
    - One display, multiple information: milage, fuel consumption, oil / coolant temperatures, ...


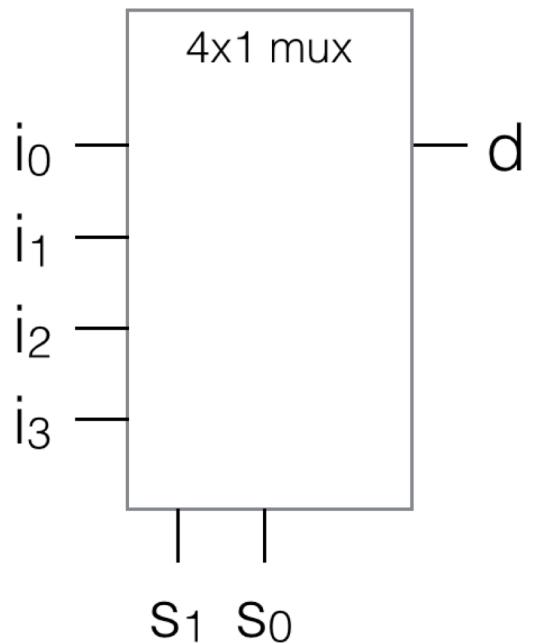
# Multiplexer

- Multiplexer is also called “**mux**”
- Has **multiple inputs** and a **single output** plus a set of select inputs
- Passes one input through to output
  - Select input value determines which output
  - Value of non-selected inputs are ignored
- Amount of select input bits determines amount of possible inputs ( $2^n$  relation, e.g. 2 select bits = 4 inputs ( $2^2$ ))


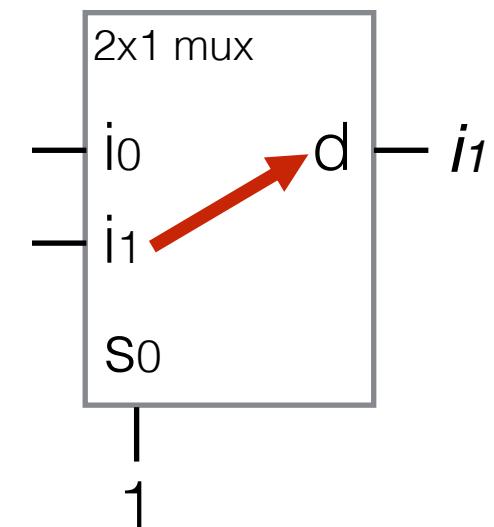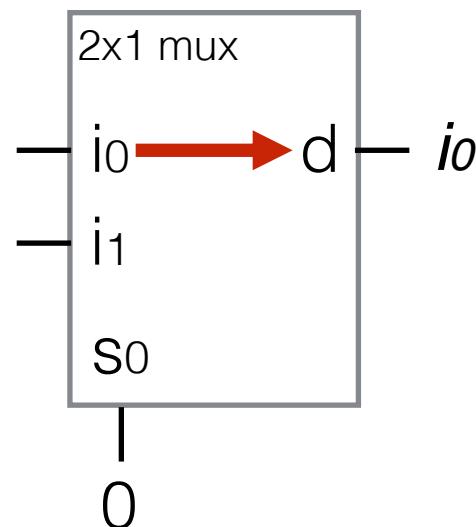
# Multiplexer

- 2x1 mux
  - If  $s_0 = 0$  input  $i_0$  is passed through to output  $d$
  - If  $s_0 = 1$  input  $i_1$  is passed through to output  $d$
  - Output  $d$  is always equal to one input ( $i_0$  or  $i_1$ )



# Multiplexer

- Similar to railyard switch:
  - Several tracks lead to one single track
  - Control lever selects which input track will connect to output track



# Multiplexer


- 2x1 mux

<b>s<sub>0</sub></b>	<b>i<sub>1</sub></b>	<b>i<sub>0</sub></b>	<b>d</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

<b>s<sub>0</sub></b>	<b>i<sub>1</sub></b>	<b>i<sub>0</sub></b>	<b>d</b>
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

# Multiplexer


- 2x1 mux

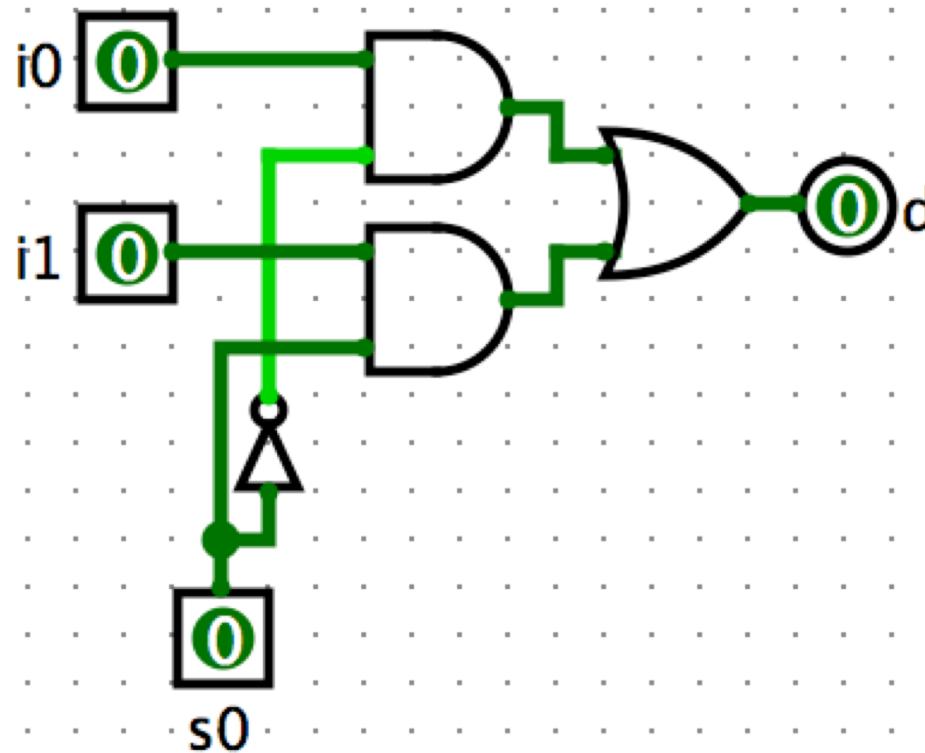

$s_0$	$i_1$	$i_0$	$d$
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

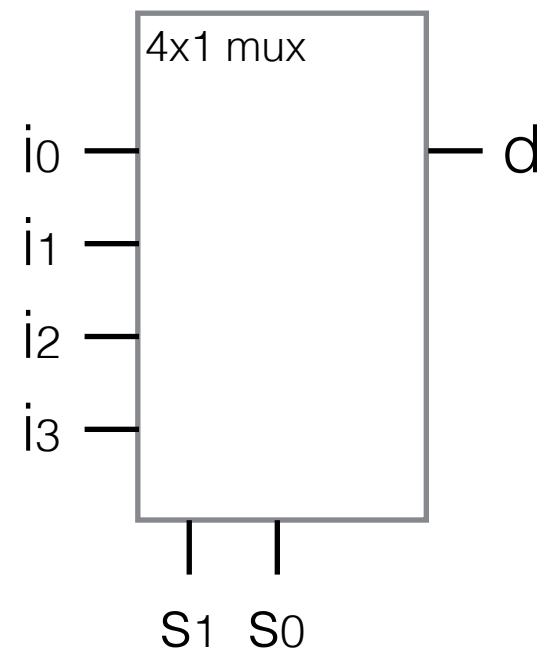
# Multiplexer

- 4x1 mux
- Binary number  $s_1s_0$  in decimal is the same as input index
  - 0b00 = 0 =  $i_0$  passed through
  - 0b01 = 1 =  $i_1$  passed through
  - 0b10 = 2 =  $i_2$  passed through
  - 0b11 = 3 =  $i_3$  passed through


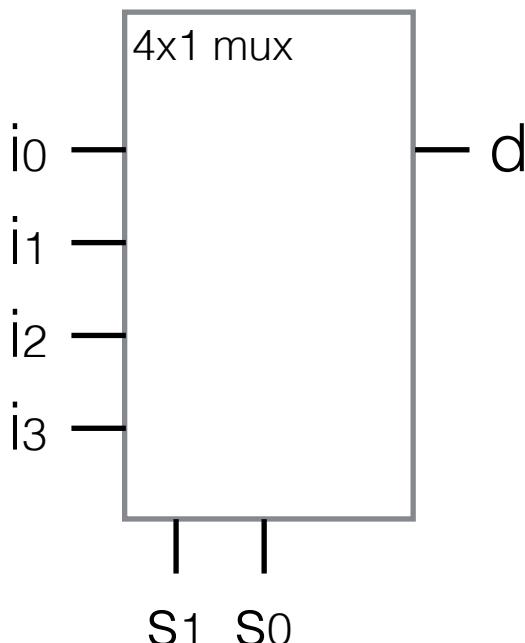
# Multiplexer

- 4x1 mux
  - 4 inputs + 2 select bits = 6 bits
  - $2^6 = 64$  rows in truth table
  - Only 8 rows needed when using *don't care* symbols




i <sub>3</sub>	i <sub>2</sub>	i <sub>1</sub>	i <sub>0</sub>	s <sub>1</sub>	s <sub>0</sub>	d
x	x	x	0	0	0	0
x	x	x	1	0	0	1
x	x	0	x	0	1	0
x	x	1	x	0	1	1
x	0	x	x	1	0	0
x	1	x	x	1	0	1
0	x	x	x	1	1	0
1	x	x	x	1	1	1

# Multiplexer


- Schematic symbol
  - Most components in Logisim have an enable pin, which can turn a component completely off (can be disabled)



2x1 mux

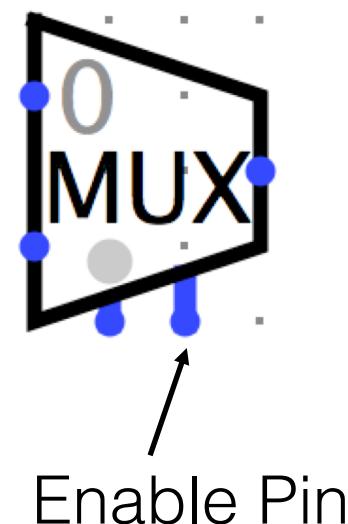

Enable Pin

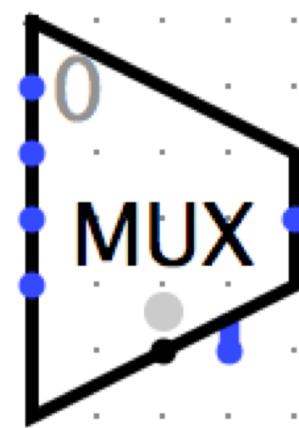

4x1 mux

# Multiplexer

- 4x1 multiplexer with input values: 0011 (i3,i2,i1,i0)
  - Select input: 01 (s1,s0) - What is the output?
    - 1 (i1 passed through)
  - Select input: 11 (s1,s0) - What is the output?
    - 0 (i3 passed through)
  - How many select inputs needed for 16x1 mux?
    - **4 select inputs** ( $16 = 2^4$ )
  - How many data inputs can a multiplexer have with five select inputs?
    - **$2^5 = 32$  data inputs**


# SER 232

Computer Systems Fundamentals I

# Topics

- Logic Component: Demultiplexer

# Demultiplexer

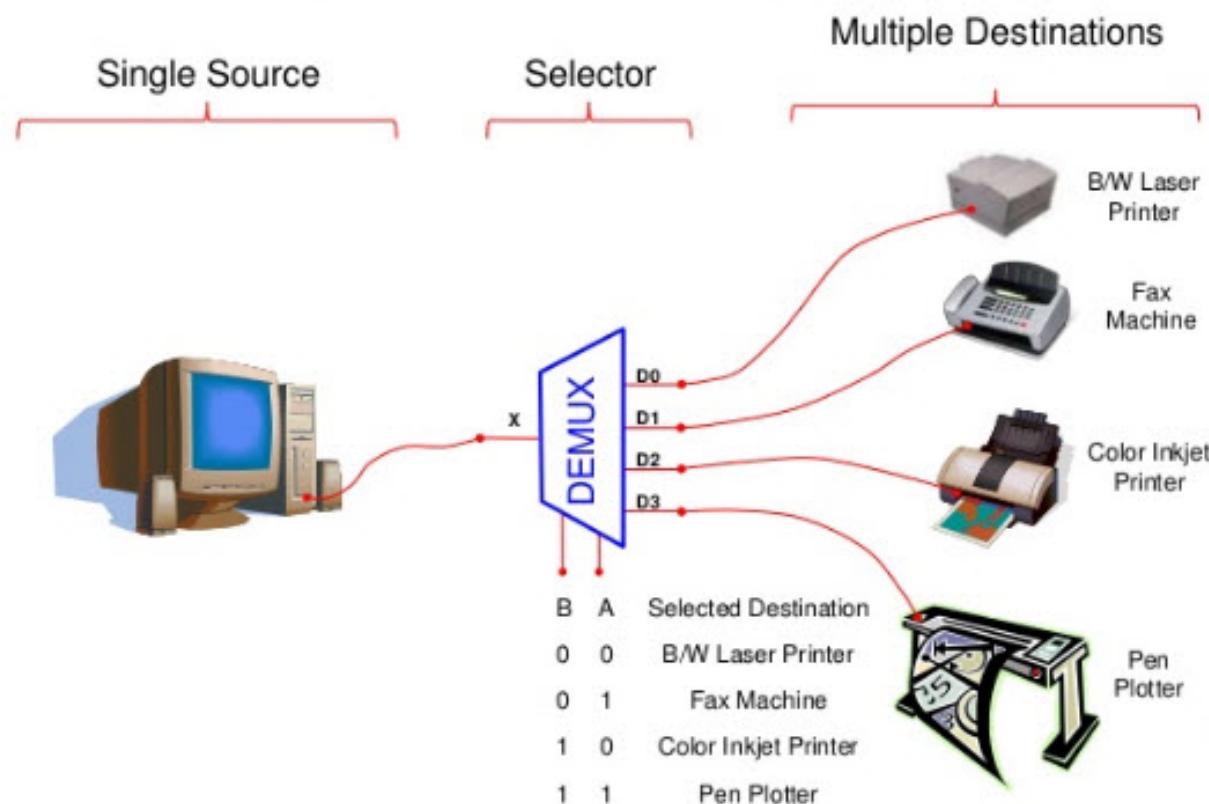


# Demultiplexer

- Single source to multiple destinations
- Analogies:
  - Different printers, plotters and/or devices that take documents as input
  - HDMI switch (console attached to TV and projector)
  - Some AV receivers support switching between different “speaker zones” (living room, kitchen, patio, bedroom, ...)



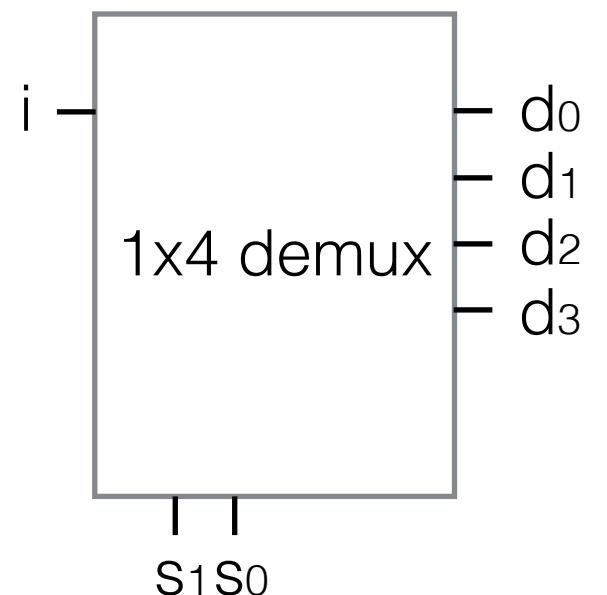
# Demultiplexer

- Demultiplexer is also called “**demux**”
- Same as mux but inputs and output swapped
  - Has **single input** and **multiple outputs**
  - Select inputs indicate which output is passed through
- Same basic behavior as multiplexer but inputs and outputs swapped


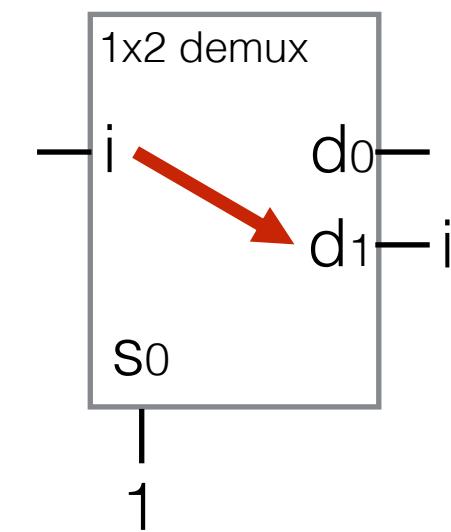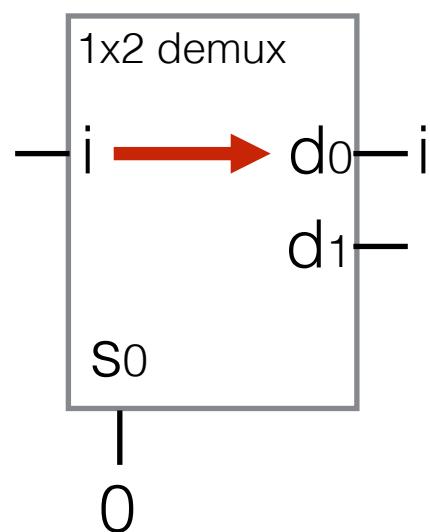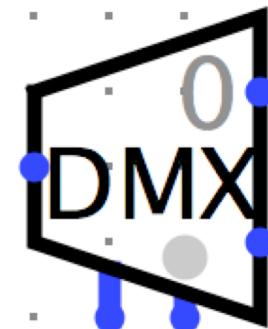
# Demultiplexer

- 1x2 demux schematic symbol (including enable pin):
- Function:
  - $s_0 = 0$ ;  $i$  is passed to  $d_0$
  - $s_0 = 1$ ;  $i$  is passed to  $d_1$




# Demultiplexer

- Also similar to railyard switch:
  - One single track splits into several tracks
  - Control lever selects which track the train will continue on



# Demultiplexer


- Circuit and truth table of 1x2 demux

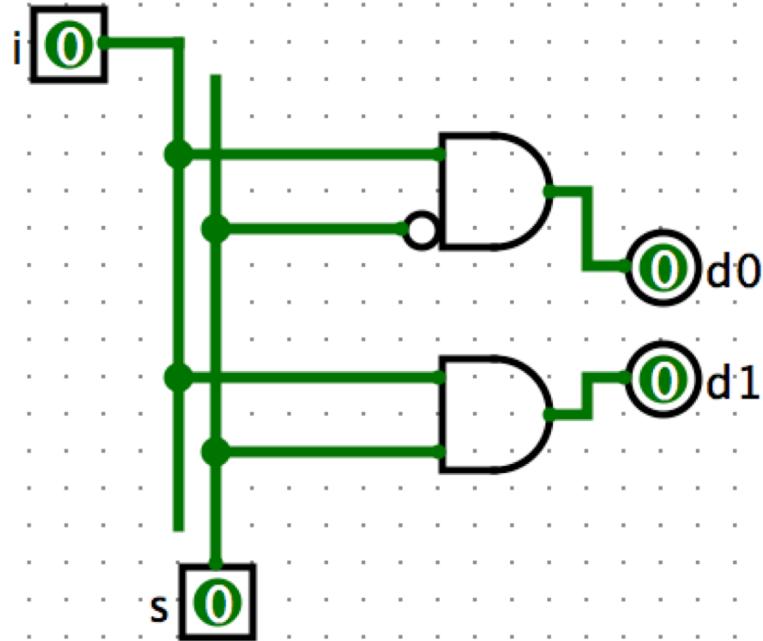

$i$	$s$	$d_1$	$d_0$
0	0	0	0
1	0	0	1
0	1	0	0
1	1	1	0
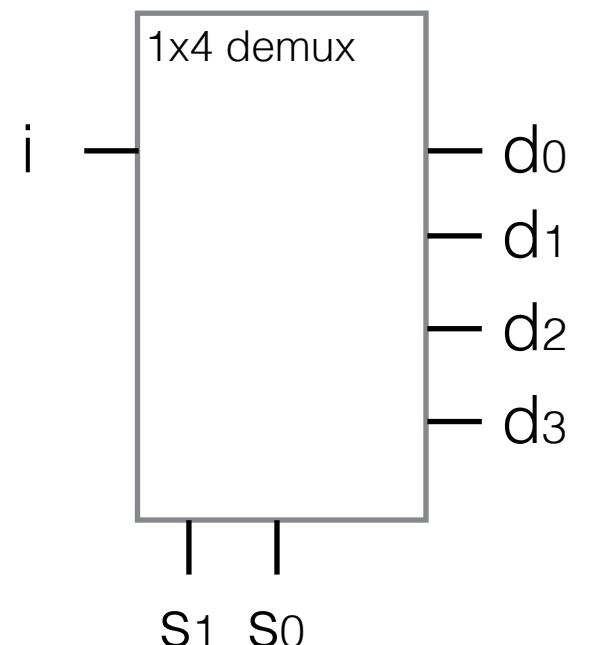
# Demultiplexer

- Binary number  $s_1s_0$  in decimal is the same as output index
- For 1x4 demux:
  - 0b00 = 0 = passed through to  $d_0$
  - 0b01 = 1 = passed through to  $d_1$
  - 0b10 = 2 = passed through to  $d_2$
  - 0b11 = 3 = passed through to  $d_3$
- Demultiplexer with  $2^n$  outputs has  $n$  select inputs



# Demultiplexer

- Truth table for a 1x4 demux

i	s1	s0	d3	d2	d1	d0
0	0	0	0	0	0	0
1	0	0	0	0	0	1
0	0	1	0	0	0	0
1	0	1	0	0	1	0
0	1	0	0	0	0	0
1	1	0	0	1	0	0
0	1	1	0	0	0	0
1	1	1	1	0	0	0

# Demultiplexer

- 1x4 demultiplexer
  - Select input: 01 ( $s_1, s_0$ ) - What is the output of  $d_2$ ?
    - **0** (input passed through to  $d_1$ , everything else is 0)
  - Select input: 11 ( $s_1, s_0$ ) - What is the output of  $d_3$ ?
    - **Value of input i** ( $i$  is passed through to  $d_3$ ,  $i=0$  then  $d=0$ ,  $i=1$  then  $d=1$ )
  - How many select inputs needed for 1x32 demultiplexer?
    - **5 select inputs** ( $32 = 2^5$ )
  - How many data outputs can a demultiplexer have with four select inputs?
    - **$2^4 = 16$  data outputs**


# SER 232

Computer Systems Fundamentals I

# Topics

- Logic Component: Encoder

# Encoder

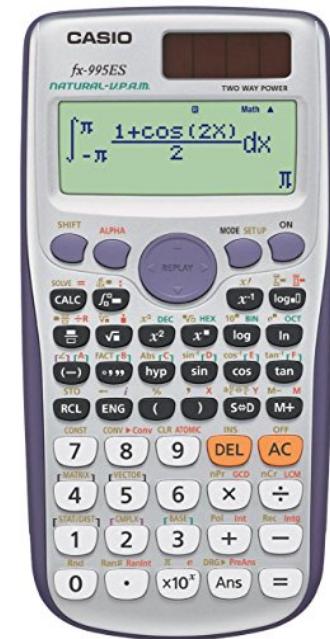


# Encoder

- A lot of connected devices can be encoded into a binary number to save pins
- Analogies:
  - Washer dial for different programs
  - Digital calculator
  - Keyboard (full size has 104 keys)

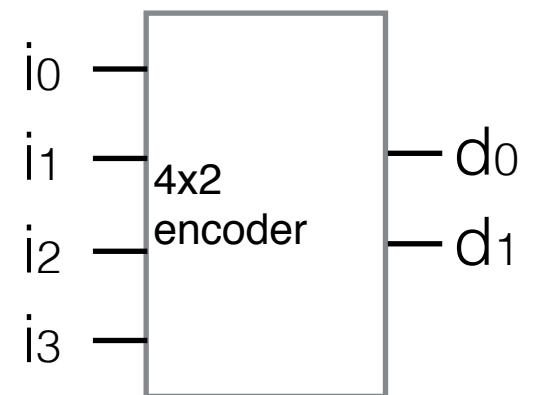
# Encoder

- **Expected:** Only one of the inputs is 1 at any given time & one input has to be 1
- Output: Binary value of input which is 1
- For  $2^n$  inputs,  $n$  outputs are needed (or:  $n$  outputs require  $2^n$  inputs)
  - $4 = 2^2$  inputs, **2** outputs
  - $8 = 2^3$  inputs, **3** outputs
- Example: 4x2 encoder


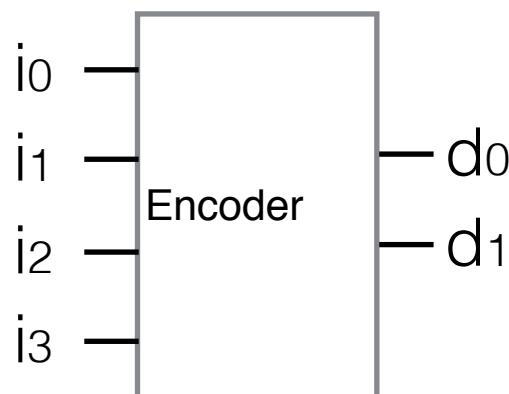
# Encoder


- Truth Table of a 4x2 encoder
  - Any other input combination would be considered invalid



$i_3$	$i_2$	$i_1$	$i_0$	$d_1$	$d_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

# Encoder

- Circuit of a 4x2 encoder

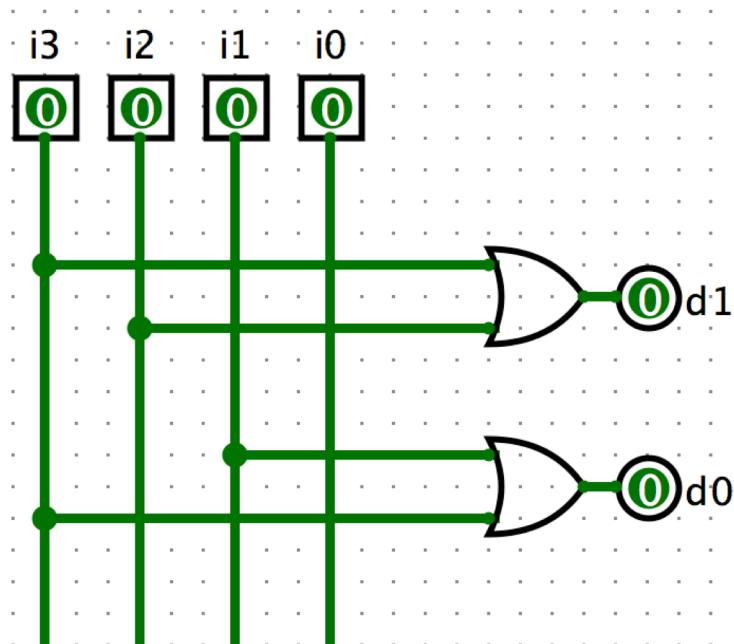

$i_3$	$i_2$	$i_1$	$i_0$	$d_1$	$d_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

# Encoder

- Truth table for 8x3 encoder
  - Only combinations listed that have defined behavior (8 rows)
- For  $2^n$  inputs, n outputs are needed
  - In this case: n = 3 ( $2^3 = 8$ , for a 8x3 encoder)

i <sub>7</sub>	i <sub>6</sub>	i <sub>5</sub>	i <sub>4</sub>	i <sub>3</sub>	i <sub>2</sub>	i <sub>1</sub>	i <sub>0</sub>	d <sub>2</sub>	d <sub>1</sub>	d <sub>0</sub>
0	0	0	0	0	0	0	<b>1</b>	0	0	0
0	0	0	0	0	0	<b>1</b>	0	0	0	1
0	0	0	0	0	<b>1</b>	0	0	0	1	0
0	0	0	0	<b>1</b>	0	0	0	0	1	1
0	0	0	<b>1</b>	0	0	0	0	1	0	0
0	0	<b>1</b>	0	0	0	0	0	1	0	1
<b>1</b>	0	0	0	0	0	0	0	1	1	1

# Encoder

- How many outputs does a 32 input encoder have?
  -
- How many outputs does a 16 input encoder have?
  -
- How many inputs does a 6 output encoder have?
  -

# Encoder

- 4x2 encoder
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 0100 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    -
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 0010 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    -
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 1111 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    -
  - Output (d<sub>1</sub>, d<sub>0</sub>) is: 00 - What is the input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>)?
    -
  - Output (d<sub>1</sub>, d<sub>0</sub>) is: 11 - What is the input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>)?
    -

# SER 232


Computer Systems Fundamentals I

# Topics

- Logic Component: Priority Encoder

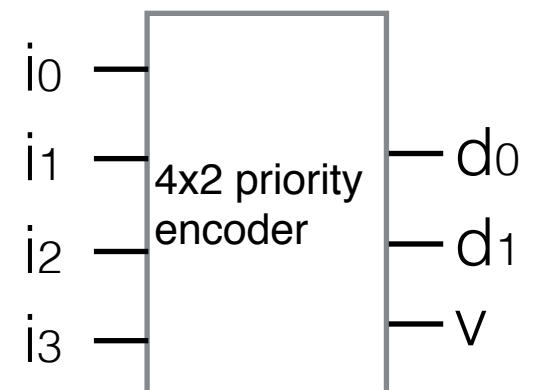
# Priority Encoder

- Input: More than one of the inputs can be 1
- Output: Binary value of input with highest number value (or bit in highest position) that is 1
- For  $2^n$  inputs,  $n$  outputs are needed
- Optional: Valid output  $v$ 
  - Indicates if at least 1 input is 1:  $v = 1$
  - If all inputs are 0 then  $v = 0$



# Priority Encoder


- Truth Table of a 4x2 priority encoder

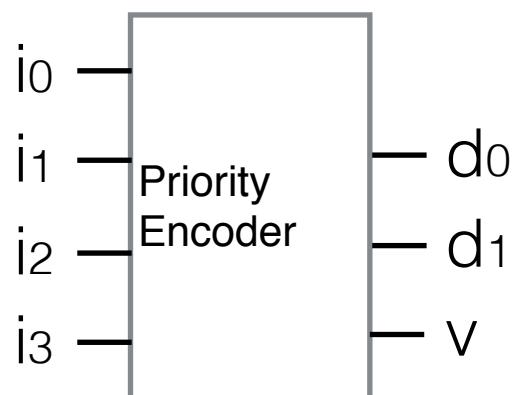

i <sub>3</sub>	i <sub>2</sub>	i <sub>1</sub>	i <sub>0</sub>	d <sub>1</sub>	d <sub>0</sub>	v
0	0	0	0	0/x	0/x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1
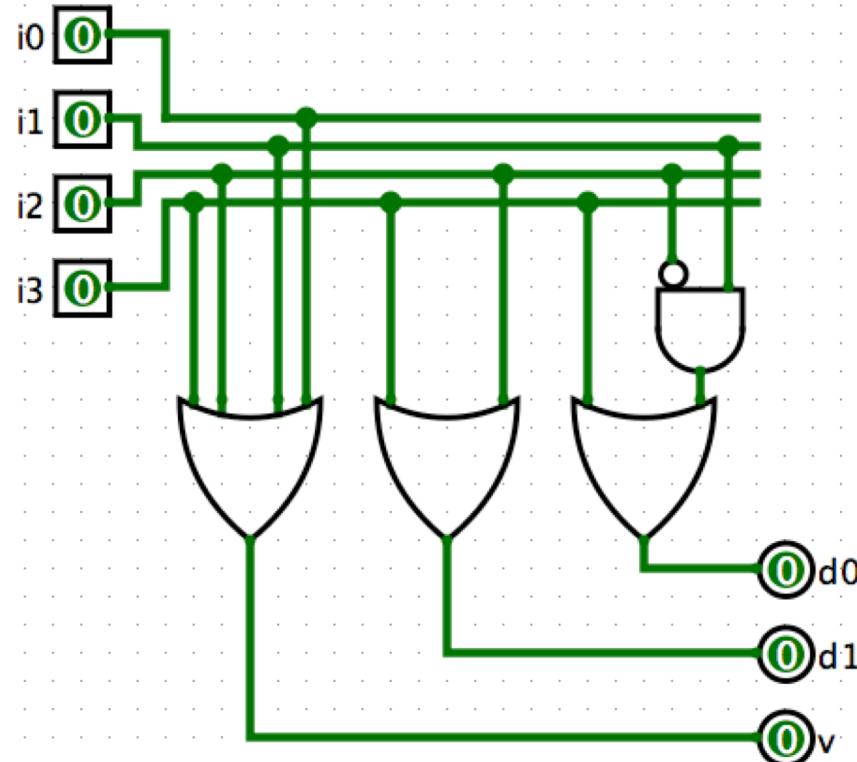
# Priority Encoder

- Circuit schematic of a 4x2 priority encoder



$i_3$	$i_2$	$i_1$	$i_0$	$d_1$	$d_0$	$v$
0	0	0	0	0/x	0/x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Priority Encoder

- 4x2 priority encoder
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 0001 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    - **00**
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 1010 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    - **11**
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 1111 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    - **11**
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 0101 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    - **10**
  - Input (i<sub>3</sub>, i<sub>2</sub>, i<sub>1</sub>, i<sub>0</sub>) is: 0100 - What is the output (d<sub>1</sub>, d<sub>0</sub>)?
    - **10**

# Priority Encoder

- 4x2 priority encoder
  - Output (d1, d0) is: 00 - What is the input (i3, i2, i1, i0)?
    - **0001**
  - Output (d1, d0) is: 01 - What is the input (i3, i2, i1, i0)?
    - **0010 or 0011; 001x**
  - Output (d1, d0) is: 10 - What is the input (i3, i2, i1, i0)?
    - **0100, 0101, 0110 or 0111; 01xx**
  - Output (d1, d0) is: 11 - What is the input (i3, i2, i1, i0)?
    - **1xxx**

# SER 232

Computer Systems Fundamentals I

# Topics

- Logic Component: Decoder

# Decoder




# Decoder

- Analogies
  - Sprinkler system zones (insufficient water pressure for all sprinklers at once requires to cycle through zones)
  - Digital New Year's Eve countdown (light up one LED out of 60 to count down seconds of last minute)
- Instead of connecting all LEDs/pumps separately with each 2 wires, binary value can be transmitted which then turns on the correct LED/pump
  - 60 LEDs can be controlled by 6 bits (60 wires vs. 12 wires)

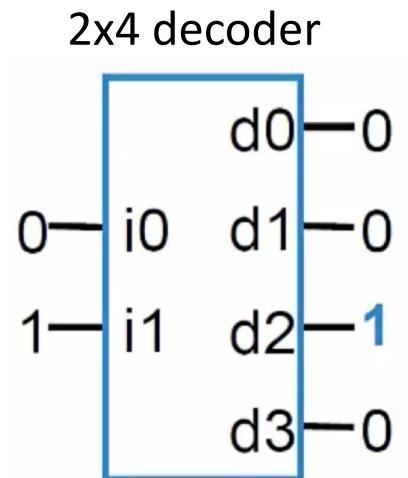
# Decoder

- Decodes an input n-bit binary number by setting exactly one of the decoder's  $2^n$  outputs to 1
  - Inputs: n inputs
  - $2^n$  outputs: The output with index equal to input value in decimal is 1
    - E.g. input value is  $0b10 = 2 =$  output d2 is 1; rest 0


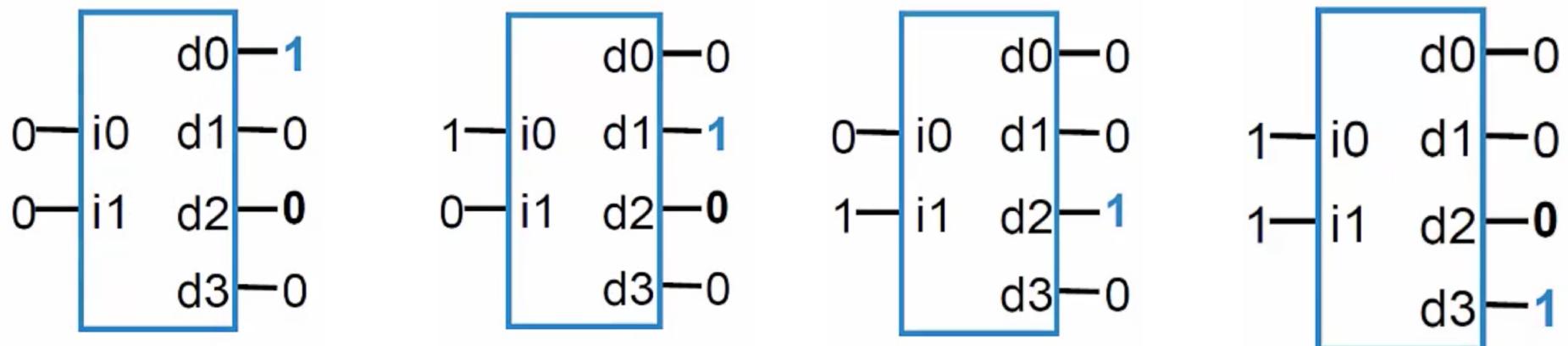
# Decoder


- Binary number on inputs indicates which output will be 1
  - 0b00 = 0; d0 = 1, rest 0
  - 0b01 = 1; d1 = 1, rest 0
  - 0b10 = 2; d2 = 1, rest 0
  - 0b11 = 3; d3 = 1, rest 0



# Decoder

- Truth table and circuit of 2x4 decoder

<b>i<sub>1</sub></b>	<b>i<sub>0</sub></b>	<b>d<sub>3</sub></b>	<b>d<sub>2</sub></b>	<b>d<sub>1</sub></b>	<b>d<sub>0</sub></b>
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

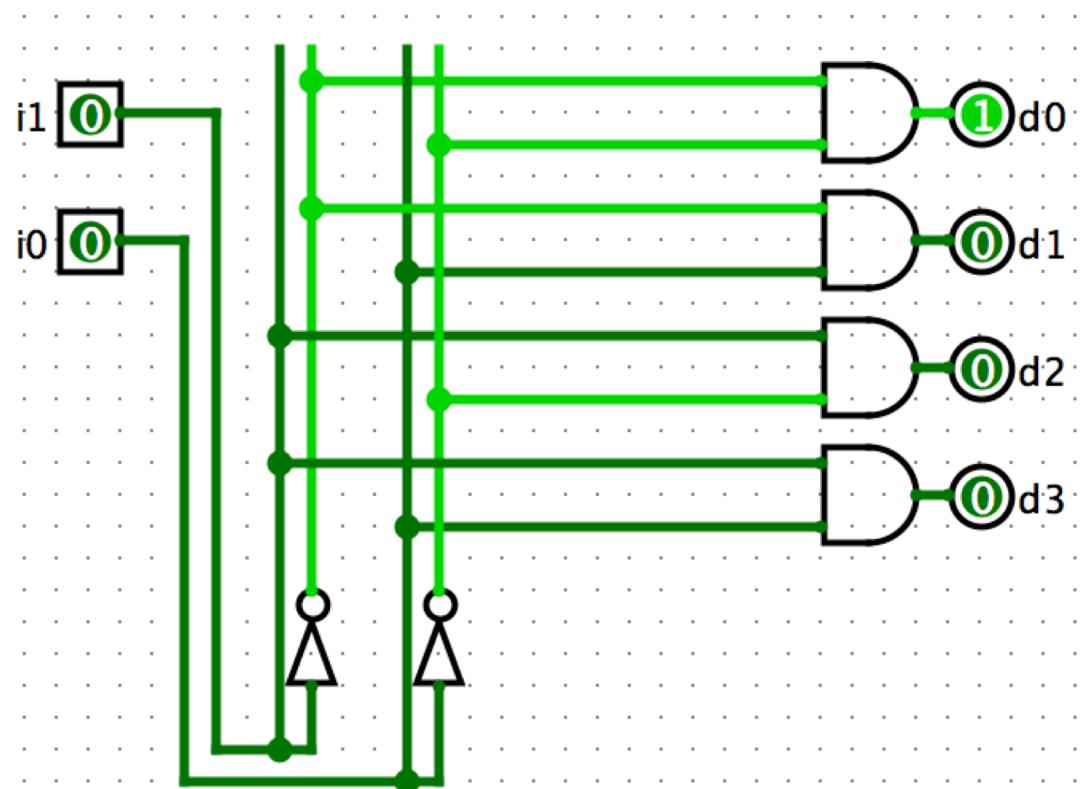

# Decoder

- Truth table for a 3x8 decoder
  - $n$  inputs,  $2^n$  outputs

<b>i<sub>2</sub></b>	<b>i<sub>1</sub></b>	<b>i<sub>0</sub></b>	<b>d<sub>7</sub></b>	<b>d<sub>6</sub></b>	<b>d<sub>5</sub></b>	<b>d<sub>4</sub></b>	<b>d<sub>3</sub></b>	<b>d<sub>2</sub></b>	<b>d<sub>1</sub></b>	<b>d<sub>0</sub></b>
0	0	0	0	0	0	0	0	0	0	<b>1</b>
0	0	1	0	0	0	0	0	0	<b>1</b>	0
0	1	0	0	0	0	0	0	<b>1</b>	0	0
0	1	1	0	0	0	0	<b>1</b>	0	0	0
1	0	0	0	0	0	<b>1</b>	0	0	0	0
1	0	1	0	0	<b>1</b>	0	0	0	0	0
1	1	0	0	<b>1</b>	0	0	0	0	0	0
1	1	1	<b>1</b>	0	0	0	0	0	0	0

# Decoder

- How many pins / wires are needed to connect 60 LEDs using a decoder?
  - **6 pins / decoder inputs** (up to 64 outputs)
- How many are needed to connect 120 LEDs using a decoder?
  - **7 pins / decoder inputs** (up to 128 outputs)
- 256 LEDs? 257 LEDs?
  - **8 pins / decoder inputs; 9 pins / decoder inputs**

# Decoder

- How many outputs does a 5 input decoder have?
  - **$2^5 = 32$  outputs**
- How many outputs does a 3 input decoder have?
  - **$2^3 = 8$  outputs**

# Decoder

- 2x4 decoder
  - Input (i<sub>1</sub>, i<sub>0</sub>) is: 00 - What is the output (d<sub>3</sub>, d<sub>2</sub>, d<sub>1</sub>, d<sub>0</sub>)?
    - **0001**
  - Input (i<sub>1</sub>, i<sub>0</sub>) is: 10 - What is the output (d<sub>3</sub>, d<sub>2</sub>, d<sub>1</sub>, d<sub>0</sub>)?
    - **0100**
  - Input (i<sub>1</sub>, i<sub>0</sub>) is: 01 - What is the output (d<sub>3</sub>, d<sub>2</sub>, d<sub>1</sub>, d<sub>0</sub>)?
    - **0010**
  - Output (d<sub>3</sub>, d<sub>2</sub>, d<sub>1</sub>, d<sub>0</sub>) is: 1000 - What is the input (i<sub>1</sub>, i<sub>0</sub>)?
    - **11**
  - Output (d<sub>3</sub>, d<sub>2</sub>, d<sub>1</sub>, d<sub>0</sub>) is: 1101 - What is the input (i<sub>1</sub>, i<sub>0</sub>)?
    - **Not defined.**