

Logic Components

Module 3

UGTA - Corey Lancelotta



Key Takeaways

CONVENTIONS

Referencing Bits & Inputs/Outputs

MULTIPLEXER

Many to One

DEMULTIPLEXER

One to Many

ENCODER

Decimal to Binary

PRIORITY ENCODER

Decimal to Binary

DECODER

Binary to Decimal

CONVENTIONS

(MSB) Most Significant Bit (bit position with the greatest value)

- 0b**1**011
- 0b**1**1110

(LSB) Least Significant Bit (bit position with the least value)

- 0b11011**0**
- 0b10110**1**

4x1 Multiplexers have **4 Inputs** and **1 Output**

1x8 Demultiplexers have **1 Input** and **8 Outputs**


8x3 Encoders have **8 Inputs** and **3 Outputs**

3x8 Decoders have **3 Inputs** and **8 Outputs**

DON'T FORGET!

1. MSB and LSB are **relative** and follow convention.
 - The **value** of the bit position dictates whether the MSB/LSB will be on the right or left.
2. When describing components:
 - The **First** number is the number of **Inputs**
 - The **Second** number is the number of **Outputs**
3. The **2ⁿ** relationship is everywhere.


MULTIPLEXER

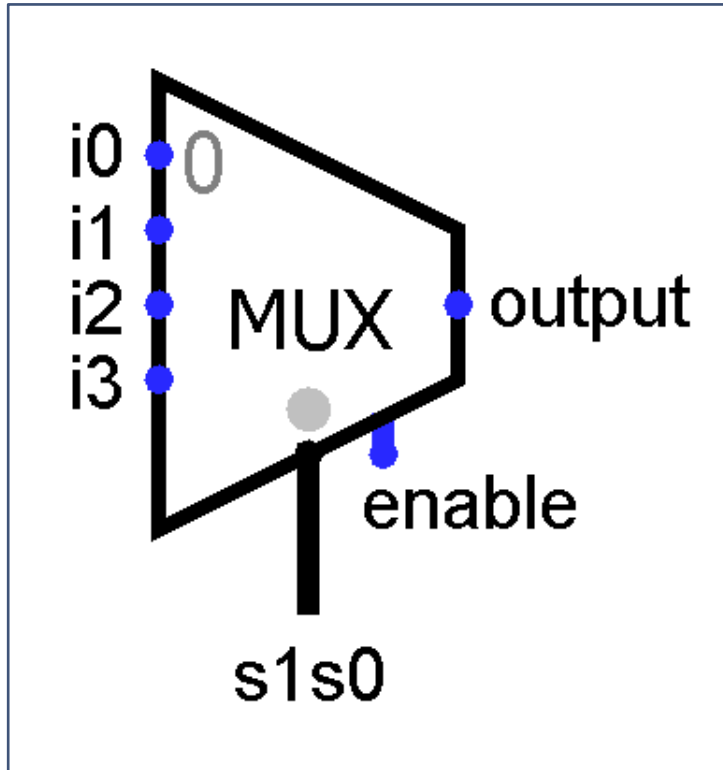

WHAT TO REMEMBER?


1. Shortened to **MUX**.
2. **Many** inputs to **One** output.
3. Uses **Select Bits** with the following relationship:
- n Select Bits allows for 2^n Inputs.
4. The **decimal value of the binary select bits** indicates which input is passed through to the output.
5. The **value** of the selected input is passed to the output.

DEMULTIPLEXER

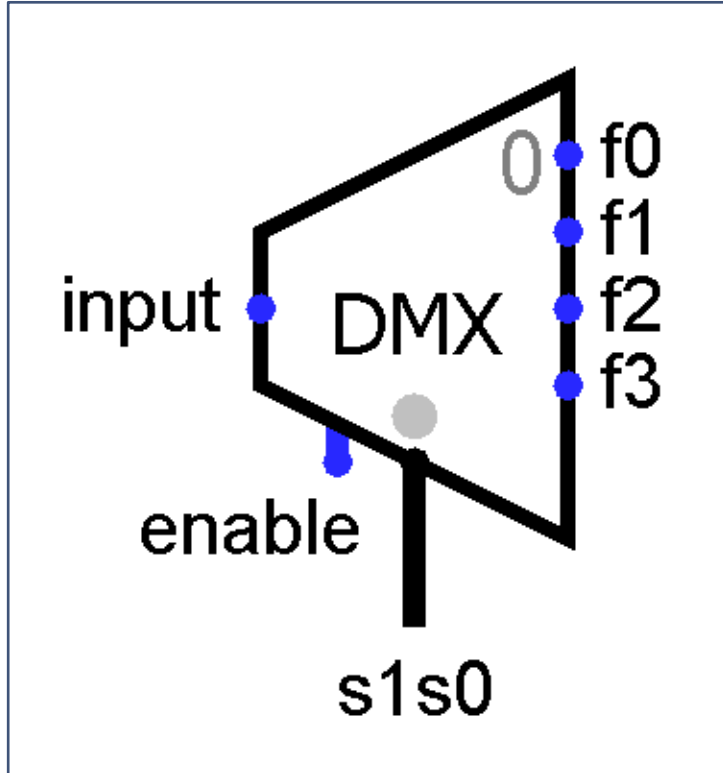


WHAT TO REMEMBER?

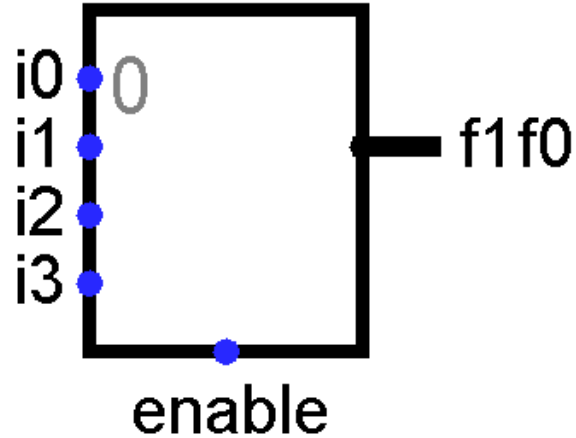1. Shortened to **DEMUX**.
2. **One** input to **Many** outputs.
3. Uses **Select Bits** with the following relationship:
- **n** Select Bits allows for **2ⁿ** Outputs.
4. The **decimal value of the binary select bits** indicates which output receives the input.
5. The **value** of the input is passed to the selected output.
6. All **non-selected outputs** have a value of **0**.




WHAT TO REMEMBER?

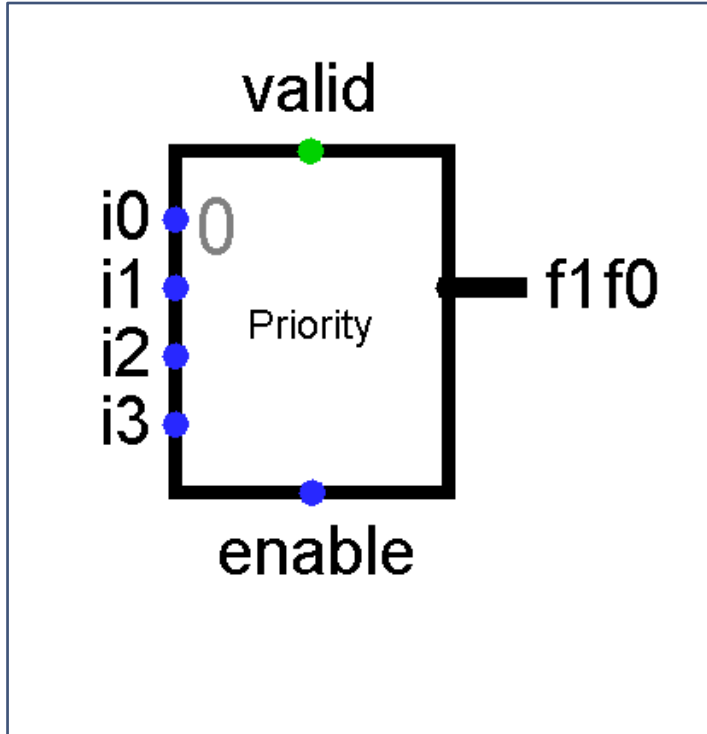1. Converts **Decimal to Binary**.
2. Does **not** use **Select Bits**.
3. The number of **Inputs/Outputs** follows the relationship:
- **n** Outputs are needed for **2^n** Inputs.
4. The **decimal index of the non-zero Input** is converted to a binary number.
5. Only **One Input** can have a value of 1 and **one of the inputs** must have a value of 1.



WHAT TO REMEMBER?

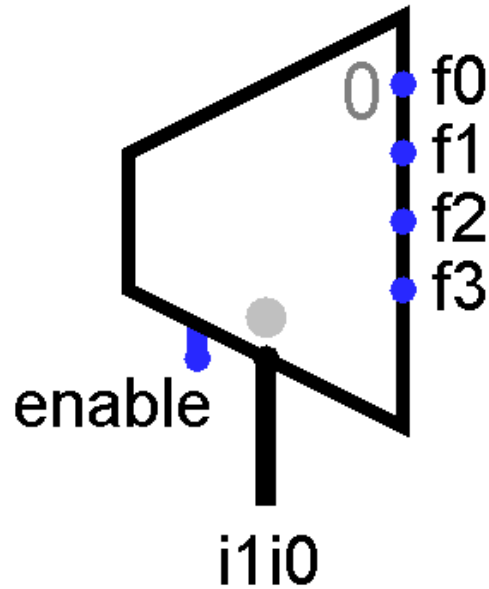1. Converts **Decimal to Binary**.
2. Does **not** use **Select Bits**.
3. The number of **Inputs/Outputs** follows the relationship:
 - **n** Outputs are needed for **2ⁿ** Inputs.
4. The **decimal index of the highest bit position input with a value of 1** is converted to a binary number.
5. **Many Inputs** can have a value of 1 and all of the inputs could have a value of 0.
6. The **Valid Bit** distinguishes between the following:
 - **All Inputs** are 0
 - **Only i0** is 1



WHAT TO REMEMBER?

1. Converts **Binary to Decimal**.
2. Does **not** use **Select Bits**.
3. The number of **Inputs/Outputs** follows the relationship:
- **n** Outputs are needed for **2^n** Inputs.
4. The **binary value of the Input** is converted to a decimal index which dictates **which Output will equal 1**.
5. **All other outputs** will have a value of **0**.



Practice Problems Questions

1. How many **Select Bits** are needed for a Multiplexer with **14 Inputs**?
2. A Multiplexer has **4 Select Bits** and we want to feed in **31 Inputs**. Is this possible?
3. How many **Select Bits** are needed for a Demultiplexer with **255 Outputs**?
4. A Demultiplexer has **6 Select Bits** and we want to send our Input to **65 Outputs**. Is this possible?
5. The **Inputs** of an Encoder are **$i_3 = 0, i_2 = 0, i_1 = 1, i_0 = 0$** . How many **Outputs** does it have and what are the **values** of the outputs?
6. The **Outputs** of an Encoder are **$f_2 = 1, f_1 = 1, f_0 = 0$** . How many **Inputs** does it have and what are the **values** of the inputs?
7. The **Inputs** of a Priority Encoder are **$i_3 = 0, i_2 = 1, i_1 = 1, i_0 = 1$** . Is this **valid**? If so, what is the **Output**? What is the **value** of the **Valid Bit**?
8. The **Inputs** of a Priority Encoder are **$i_3 = 0, i_2 = 0, i_1 = 0, i_0 = 1$** . Is this **valid**? If so, what is the **Output**? What is the **value** of the **Valid Bit**?
9. You need to decode the number **0b1011**. Identify the values of the **A** and **B** for the **AxB** Decoder that you would use.
10. The **Outputs** of a Decoder are **$f_3 = 0, f_2 = 0, f_1 = 0, f_0 = 1$** . What was the **Input**?



Practice Problems **Answers**

1. 3 Select Bits can support 8 Inputs and 4 Select Bits can support 16 Inputs. Therefore, **we need at least 4 Select Bits**.
2. 4 Select Bits can only support 16 Inputs. Therefore, **we can't support 31 Inputs**.
3. 7 Select Bits can support 128 Outputs and 8 Select Bits can support 256 Outputs. Therefore, **we need 8 Select Bits**.
4. 6 Select Bits can only support 64 Outputs. Therefore, **we can't support 65 Outputs**.
5. In order to encode 4 decimal numbers, **we need 2 outputs**. We are encoding the decimal number 1 (**since $i_1 = 1$**) into binary, so the output will be **$f_1f_0 = 01$** .
6. This Encoder is outputting a 3-Bit binary number. Therefore, we can encode 8 values and thus it has **8 Inputs**. Since we encoded the decimal value of 6, the inputs would be **$i_7 = 0, i_6 = 1, i_5 = 0, i_4 = 0, i_3 = 0, i_2 = 0, i_1 = 0, i_0 = 0$** .
7. A Priority Encoder can receive multiple inputs with a value of 1, so **this is valid** and the valid bit would be **$v = 1$** . We are encoding the highest decimal-valued bit that has a value of 1, so we encode the decimal value 2 (**since $i_2 = 1$**) into binary. Therefore, the output is **$f_1f_0 = 10$** .
8. Yes, **this is valid** and the valid bit is **$v = 1$** . We are encoding the decimal value 0 (**since $i_0 = 1$**) into binary. Therefore, the output is **$f_1f_0 = 00$** .
9. We have a 4-Bit binary number. This means we need 16 outputs to cover all possible decimal values. Thus, we have a **4x16 Decoder**.
10. The output of a Decoder is the decimal representation of the binary number that was decoded. Our output is the decimal value 0, so our input must have been **$i_1i_0 = 00$** .